

Smart Blind Stick - How To Wire It Up

A simple picture guide: every part connects to the Brain (the Arduino)

How to read the wires

- **Red = POWER (5V)** - gives the part electricity
- **Black = GROUND (GND)** - the return path
- **Blue = SIGNAL** - carries the message to the Brain


Tip: VCC means "power in". The arrow shows which Arduino pin to use.

★ The Golden Rule

Almost every part connects the SAME 3 ways:

- 1) VCC or + → **5V** (power)
- 2) GND or - → **GND** (ground)
- 3) one **Signal** wire → its own Arduino pin

Get these 3 right and the part works!

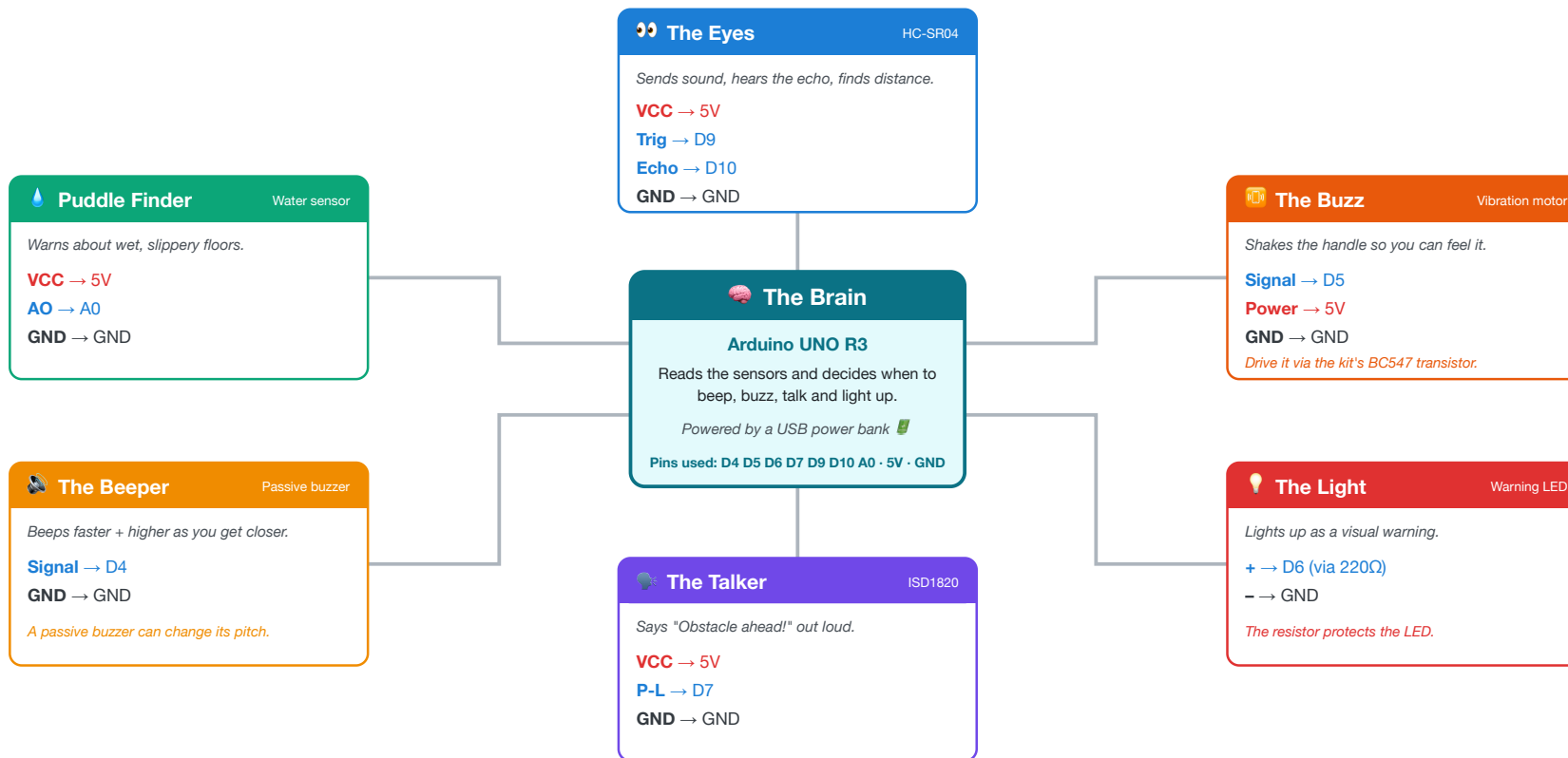

Building tips (read me!)

- Use the breadboard's **RED (+)** strip for all 5V wires, and the **BLUE (-)** strip for all GND wires.
- Match the signal pins exactly: Eyes Trig=D9 · Echo=D10 · Beeper=D4 · Buzz=D5 · Light=D6 · Talker=D7 · Puddle=A0.
- Remember the Golden Rule: every part also needs **5V** (power) and **GND** (ground).
- Power the whole stick from a USB power bank into the Arduino's USB port.
- New to Arduino? Watch the beginner video linked in the Implementation Guide first. 📺